

Analog Electronics

Laboratory exercise 3

Fall 2016

1 Abstract

In this experimentation using the information that was learned through lecture, we will design and construct our first Operational Amplifier. This amplifier will be designed in Multi-Sim 13, and the majority of our calculations and testings will also be in Multi-Sim. These amplifiers we design will be have a gain of $A_v = -10$ and $A_v = -100$ respectively. Once the designed amplifier meets all the design constraints, we will construct it using the given 741 op-amp and using our work bench tools; such as our occiloscope, function generator, multimeter, and our power supply. Once the circuit is constructed we then will test its various inputs and outputs to ensure our given A_v 's were met.


2 Theory

Multi-Sim is one of the most powerful tools an electrical engineer has at there disposal. By being able to create and test a circuit before spending time & resources constructing it, we can work out problems before hand and ensure our specifications are met. By designing two amplifiers we can better understand the importance of our resistor values and there effect on our gain, A_v .

3 Experimentation

This experimentation will use two variations of the following circuit for our gain of $A_v = -10$ and $A_v = -100$ respectively.

Figure 1: overview design of our Amplifier

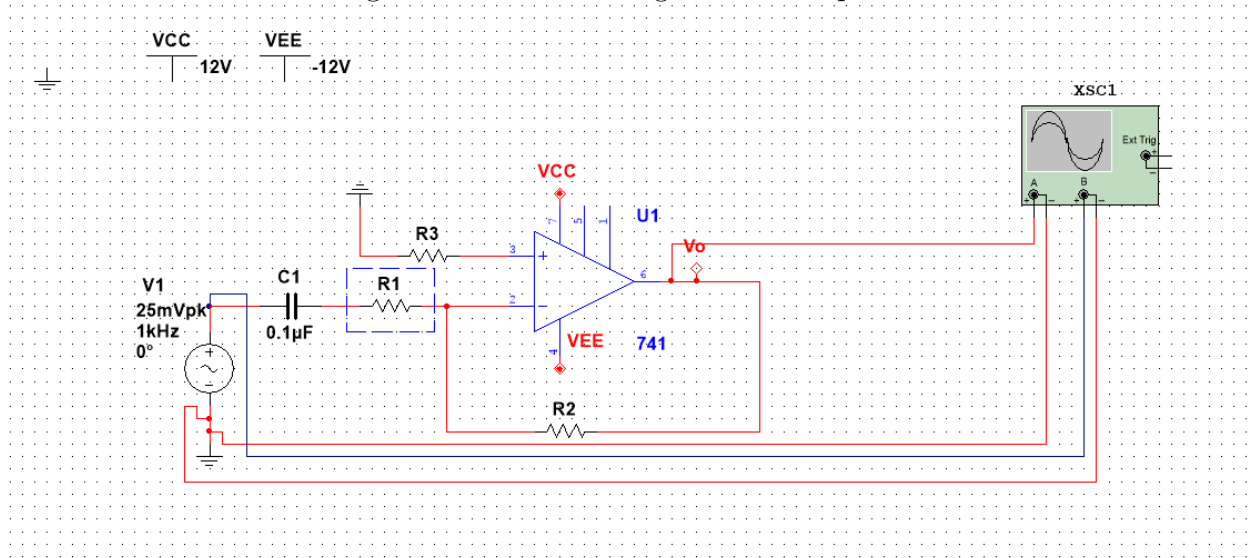

Our first circuit $A_v = -10$ will use the following resistance values

$$R_1 = R_3 = 1k\Omega, R_2 = 10k\Omega$$

Our Second circuit $A_v = -100$ will use the following resistance values

$$R_1 = R_3 = 1k\Omega, R_2 = 100k\Omega$$

To power our op-amp we will utilize the above schematic as reference. Do not apply voltage yet.

3.1 Measuring AC Gain

1. Gather a $100k\Omega$, $10k\Omega$, $.1\mu F$ capacitor, and two $1k\Omega$. Measure and log there values with the multimeter. These will be used for both circuits.
2. Using Figure 1 and the $A_v = -10$ resistor values, place the resistors and capacitor onto the circuit board.
3. Ensure that the resistors and capacitors go to the correct pins on our Op-Amp
4. Power the DC voltage source on.
5. Using the DMM measure the voltage with respect to ground of the input, output, and inverting terminals. Log this data.
6. Attach the function generator probes to the points shown in the schematic, using the given value. Power it on.
7. Attach the oscilloscope to the points as shown in figure 1.
8. Measure the input and output waveforms using the oscilloscope, ensuring that DC power source is on.
9. Log these values with your data.

3.2 Measuring DC gain

Now that we measured the AC gain we can do the same for DC, to do so we must first rearrange the circuit.

1. First remove the capacitor, as it will cause a short circuit when used in junction with a DC source.
2. Replace the function generator with a $-1v$ DC voltage from the bench power supply.
3. Using the DMM measure the output voltage from $-1v$ to $1v$ on intervals of $.2v$
4. Log this data into your table.

For the second circuit with a gain of -100 replace the resistance values and repeat steps 2-4 in section 3.2 with a voltage of $-0.1v$ to $0.1v$ by intervals of $0.02v$

3.3 Measurements

To calculate our gain we will compare our V_i from our function generator to our V_o on our oscilloscope. From these two values we can calculate the A_v , or gain.

$$A_v = \frac{V_o}{V_i}$$

When we plug our values in we get

$$A_v = \frac{V_o}{V_i} = \frac{830mV}{90mV} = 9.2$$

The AC gain for amplifier is ≈ 9

By replace the function generator with a $-1v$ DC voltage from the bench power supply. And using the DMM measure the output voltage from $-1v$ to $1v$ on intervals of $.2v$, we get the following table

Table 1: $A_v = -10$	
Input Dc Voltage	Output Voltage
-1	10.04
-0.8	8.03
-0.6	6.03
-0.4	4.02
-0.2	2.01
0	0.006
0.2	-2
0.4	-4.01
0.6	-6.02
0.8	-8.02
1	-10.03

We can now calculate our DC voltage gain.

$$A_v = \frac{V_o}{V_i} = \frac{10.04V}{-1V} = -10.04$$

The DC gain for the amplifier is ≈ 10

By doing the same as the previous table, but with our $A_v = -100$ circuit we get this table.

Table 2: $A_v = -100$

Input Dc Voltage	Output Voltage
-0.1	10.14
-0.08	8.13
-0.06	6.11
-0.04	4.1
-0.02	2.09
0	0.081
0.02	-1.9
0.04	-3.9
0.06	-5.98
0.08	-8
0.1	-10.01

We can now calculate our DC voltage gain.

$$A_v = \frac{V_o}{V_i} = \frac{10.1V}{-0.1V} = 101$$

The DC gain for the amplifier is ≈ 101

4 Conclusion

In this experimentation we used a variety of analysis techniques to calculate and create two amplifiers that successfully took our input voltage and amplified it to a desired output voltage. During the lab several problems arose due to my lack of experience with these circuits. The first problem was the wiring of DC power supply to both +12v and -12v. Once I understood how the DMM creates relative voltage I was able to easily fix the problem and ensure it won't happen again. Another problem I ran into was I created a fractional amplifier on accident by mixing up my R_1 and R_2 resistors. Although unintentional, it helped shape my understanding of a resistor's effect on an operational amplifier. The measurements that were taken in practice although close, were not exactly what the multi-sim predicted. This is due to the fact that Multi-sim is just that, a simulation. There are many factors that affect our reading in the real world and resistor tolerances are just one of them.